

National Exams December 2002

98-Elec-A1 Circuits


3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumptions made;
  2. Candidates may use one of two calculators, a Casio FX-991 or Sharp EL-540. This is a closed-book examination. A short table of Laplace transforms is included.
  - 3.. Any *five* questions constitute a complete paper. Only the *first five* questions as they appear in your answer book will be marked.
  4. All questions are of equal value.
- 

... continued on page 2

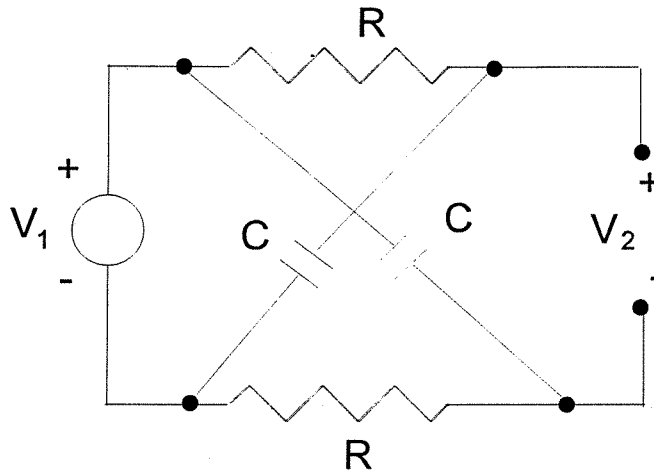1. (a) Write the node voltage equations for the RC-lattice network shown below, and use them to derive the transfer function  $\frac{V_2(s)}{V_1(s)}$  if  $R = 10 \text{ M}\Omega$  and  $C = 0.1 \text{ }\mu\text{F}$ .



- (b) Determine the response of this network to a unit impulse.

- 2 The transfer function of a network is given by

$$\frac{V_2(s)}{V_1(s)} = \frac{24(s^2 + 6s + 25)}{(s + 3)(s^2 + 4s + 5)}$$


- (a) Determine  $v_2(t)$  if  $v_1(t)$  is a unit step, assuming zero initial conditions.

- (b) Determine the steady-state component of  $v_2(t)$  if

$$v_1(t) = 5 + 3 \cos\left(2t + \frac{\pi}{3}\right).$$

... continued on page 3

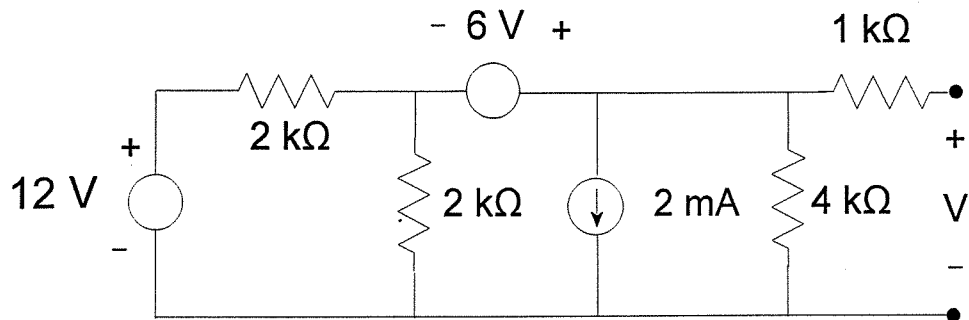3. A network with two voltage sources, and a current source is shown below.



- (a) Determine the Thevenin equivalent circuit at the two terminals emerging from the network.
- (b) What should be the value of the load connected at these terminals so that the maximum possible power is delivered to this load?
- (c) What will be the value of this maximum power?
4. The Laplace transform of the function  $f(t)$  is given by

$$F(s) = \frac{15(s+2)(s+4)}{(s+3)(s^2+4s+20)}$$

Determine the Laplace transform of each of the following


(a)  $e^{-3t}f(t)$ , (b)  $tf(t)$ , (c)  $\frac{df}{dt}$ .

5. Determine the inverse Laplace transform of each of the following:


(a)  $\frac{12(s+2)}{s(s+1)^2}$ , (b)  $\frac{10(s+1)}{(s+2)(s^2+2s+2)}$

...continued on page 4

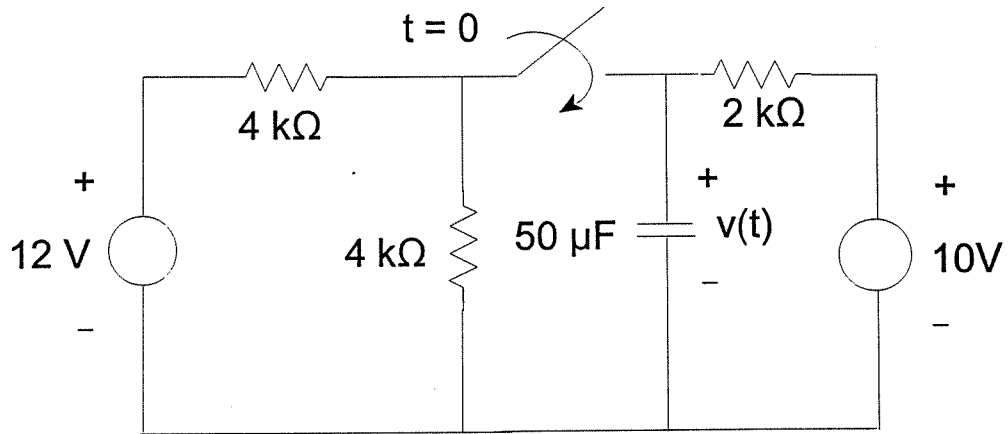6. In the network shown below, the switch is closed at  $t = 0$ . Determine,  $v(t)$ , the voltage across the capacitor for  $t \geq 0$  if it is known that  $v(0) = 5$  volts.



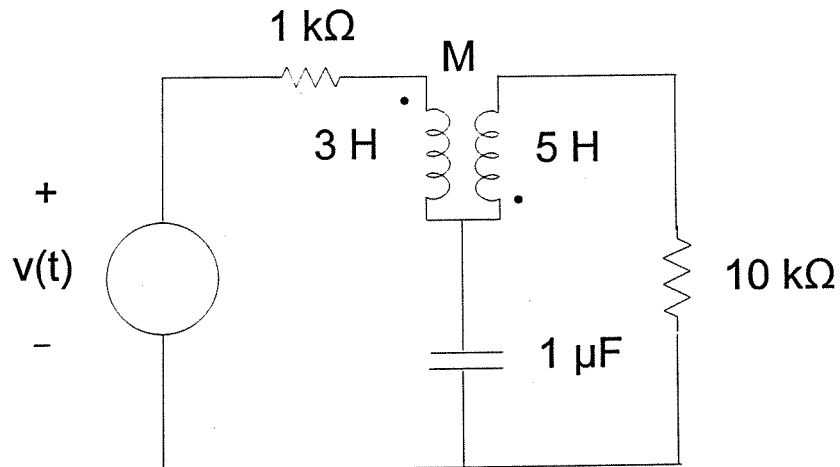7. In the network shown below, the mutual inductance  $M$  between the coils is  $2\text{ H}$  and the applied voltage is given by  $v = 100 \cos 1000t$ . Determine the steady-state voltage across the  $10\text{ k}\Omega$  resistor.



END

## A SHORT TABLE OF LAPLACE TRANSFORMS

$f(t)$	$F(s)$	$f(t)$	$F(s)$
unit impulse	1	$\sin \beta t$	$\frac{\beta}{s^2 + \beta^2}$
unit step	$\frac{1}{s}$	$e^{-\alpha t} \cos \beta t$	$\frac{s + \alpha}{(s + \alpha)^2 + \beta^2}$
$e^{-\alpha t}$	$\frac{1}{s + \alpha}$	$e^{-\alpha t} \sin \beta t$	$\frac{\beta}{(s + \alpha)^2 + \beta^2}$
$t$	$\frac{1}{s^2}$	$tf(t)$	$-\frac{dF(s)}{ds}$
$\cos \beta t$	$\frac{s}{s^2 + \beta^2}$		

## INVERSE LAPLACE TRANSFORMATION

Given any proper rational function  $F(s)$ , perform partial fraction expansion by evaluating residues at the various poles. Inverse Laplace transform for each term can now be obtained using the following table,

$F(s)$	$f(t)$
$\frac{A}{s + \alpha}$	$Ae^{-\alpha t}$
$\frac{C + jD}{s + \alpha + j\beta} + \frac{C - jD}{s + \alpha - j\beta}$	$e^{-\alpha t}(2C \cos \beta t + 2D \sin \beta t)$
$\frac{A}{(s + \alpha)^{n+1}}$	$\frac{At^n e^{-\alpha t}}{n!}$
$\frac{C + jD}{(s + \alpha + j\beta)^{n+1}} + \frac{C - jD}{(s + \alpha - j\beta)^{n+1}}$	$\frac{2t^n e^{-\alpha t}}{n!}(C \cos \beta t + D \sin \beta t)$