

National Examinations, December 2002

**98-Elec-B1, Advanced Circuits Analysis and Design**

**3 hours duration**

**NOTES:**

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumptions made.
2. Candidates may use one of the approved Casio or Sharp calculators. No programmable calculators are allowed. This is a closed-book examination.
3. Any five questions constitute a complete paper. Only the first five questions, as they appear in your answer book, will be marked.
4. All questions are of equal value; part marks are also indicated.
5. Refer to the appendix for extra information.


**Question 1:**

In figure-1, the switch was open for a long time. At  $t=0$ , the switch is closed. Using a differential equation approach, (a) write the differential equation involving  $v_o(t)$ .

[10]

(b) Solve the differential equation to find the output voltage,  $v_o(t)$  for  $t > 0$ .

[10]

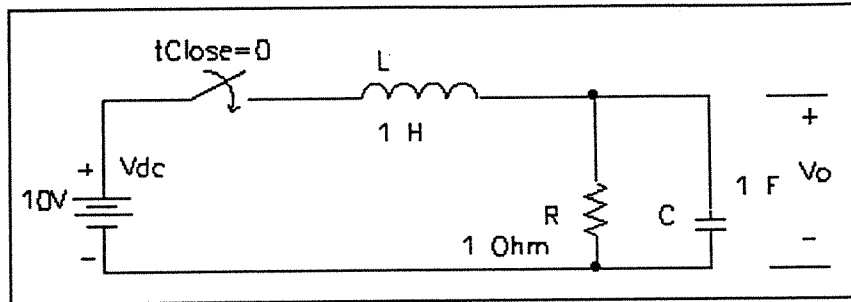


**Figure-1**

**Question 2:**

(a) Obtain the transfer function,  $T(s) = \frac{Y(s)}{X(s)}$  of the following signal flow block diagram.

[10]

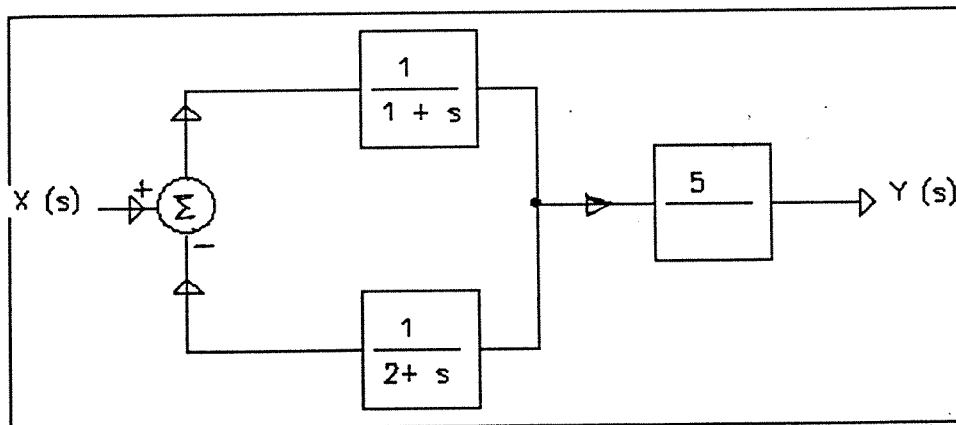

**Figure-2**

(b) Plot the poles and the zeros of the transfer function, and from the locations of the poles and zeros, state whether the system will be stable and what type of transient time response the output will display.

[10]

**Question 3:**

If the transfer function of a circuit is

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{5000(s+1)}{s(s+10)(s+50)},$$

(a) draw the Bode plot (amplitude and phase), showing clearly the break frequencies. Please use the graph paper provided in the appendix. [12]

(b) If  $v_{in}(t) = 10 \cos 200t$ , calculate  $v_o(t)$ . [8]

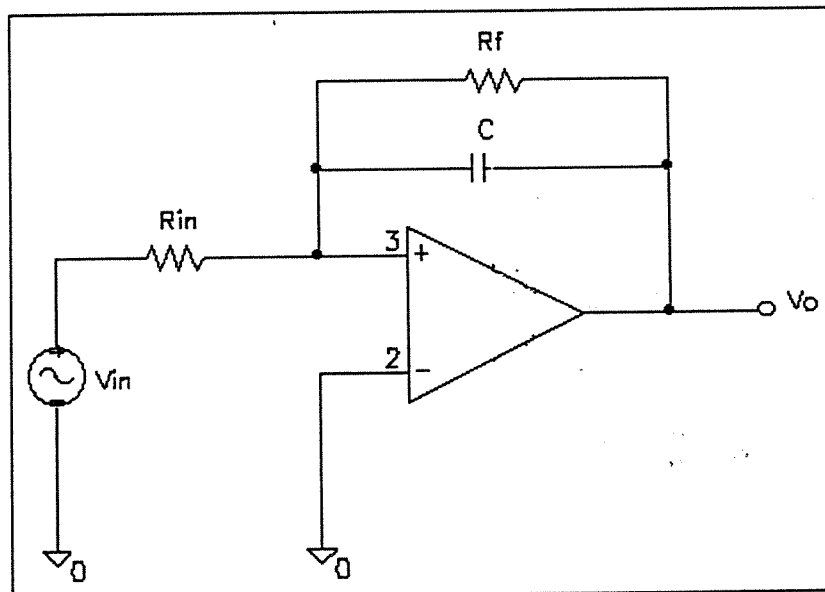
**Question-4:**

Figure -3

Figure -3 shows a circuit with an opamp.

(a) Derive an expression of its transfer function


$H(s)$  in terms of  $C$ ,  $R_f$  and  $R_{in}$ . [10]

(b) If  $C = 1 \mu\text{F}$ ,  $R_f = 10 \text{ k}\Omega$  and  $R_{in} = 1 \text{ k}\Omega$ , calculate its cutoff frequency,  $f_c$ . [5]

(c) Sketch its Bode (amplitude) plot, and from this plot, state what type of filter this circuit will perform. [5]

**Question 5:**


Obtain the transfer function,  $H(s)$  of a Butterworth filter to approximate the following 'Brickwall' specifications.

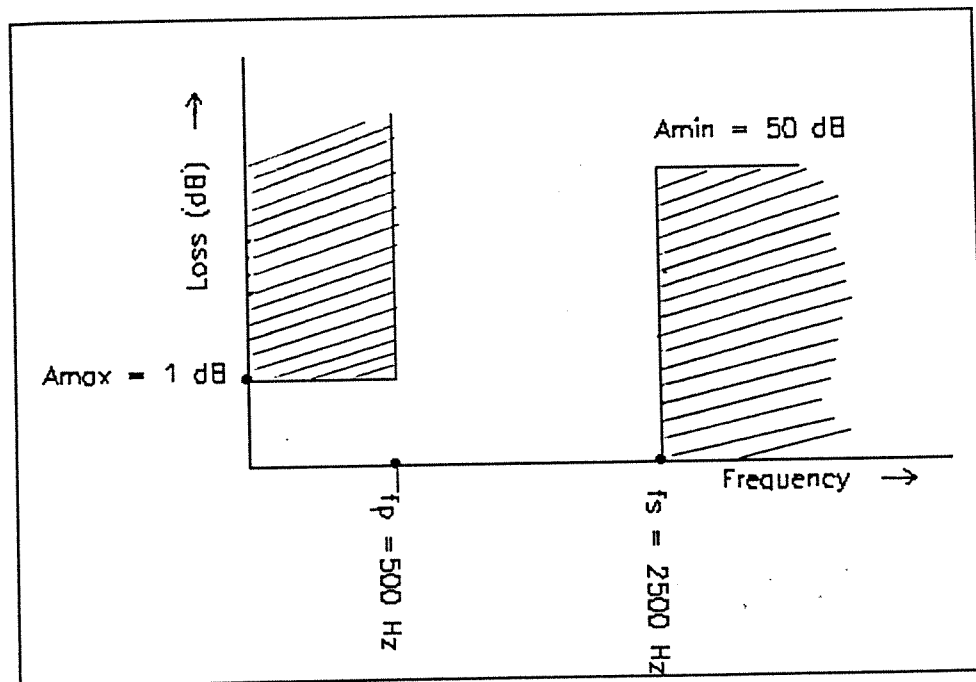**Figure 4**

The relevant filter equations are provided in the appendix.


**[20]**

**Question 6:**

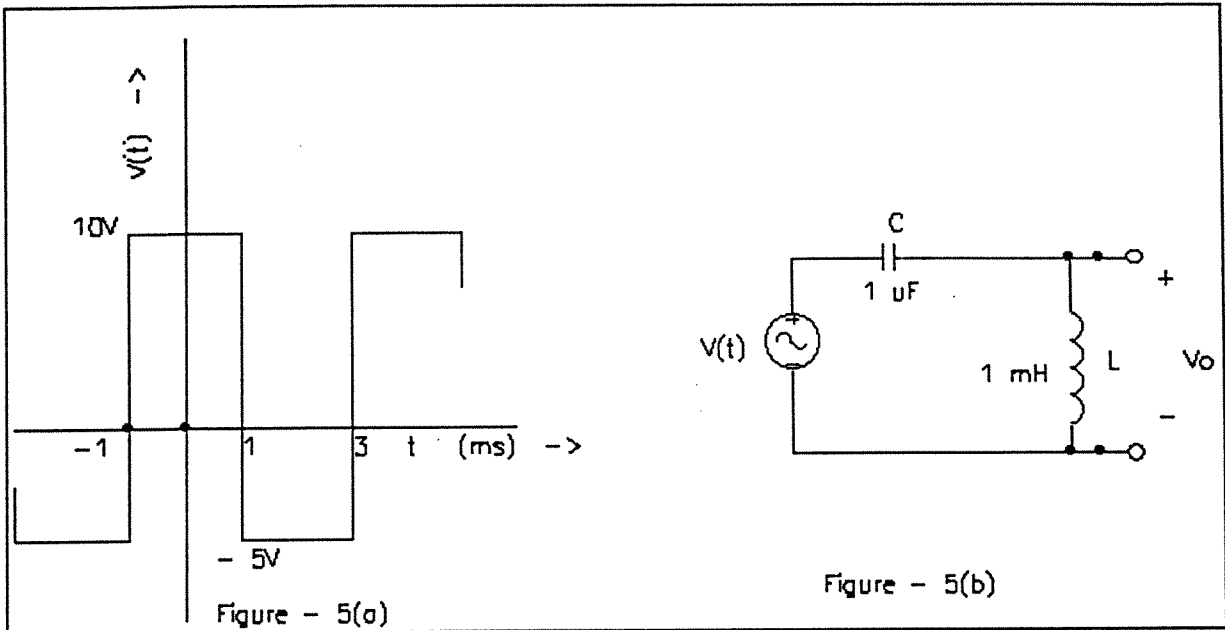

- (i) For the waveform of  $V(t)$  shown in Figure –5(a), calculate its frequency components upto the 3<sup>rd</sup> harmonics. [10]
- (ii) If  $V(t)$  is applied to the circuit shown in Figure – 5(b), calculate its output voltage  $V_o$  due to the 3<sup>rd</sup> harmonic. [10]

**Question 7:**

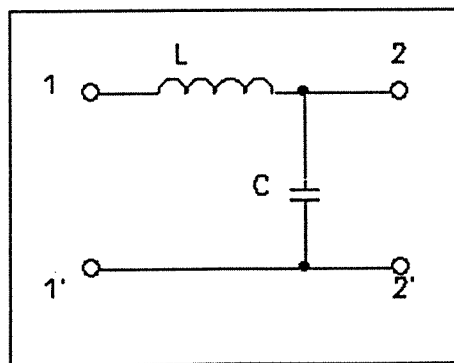

**Figure-6**

- Figure-6 shows a two-port network. (a) Calculate its [T] – transmission line parameters. [10]
- (b) If two of the L-sections of lines are connected in cascade i.e. one section connected to the next section, calculate its overall [T] parameters. [10]

**Question 8:**

A transmission line has the following parameters at 1.5 GHz:

$$L = 10 \text{ nH/m} \quad R = 1 \text{ } \Omega/\text{m} \quad G = 0.25 \times 10^{-3} \text{ mho/m} \quad C = 0.2 \text{ pF/m}$$

- Calculate (i) the Characteristic impedance of the line,  
(ii) the propagation constant,  
(iii) the load impedance to eliminate the reflection from the load.  
(iv) if the line is terminated with a load impedance of  $100 - j 50$  Ohms,  
calculate its reflection coefficient, and the standing wave ratio. [20]

Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
Ku(t)		K / s
e <sup>-at</sup> u(t)		1 / (s+a)
sin wt . u(t)		w / (s <sup>2</sup> +w <sup>2</sup> )
cos wt . u(t)		s / (s <sup>2</sup> +w <sup>2</sup> )
$\frac{df(t)}{dt}$		s F(s) - f(0 <sup>-</sup> )
$\frac{d^2 f(t)}{dt^2}$		s <sup>2</sup> F(s) - s f(0 <sup>-</sup> ) - f'(0 <sup>-</sup> )
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$

---

**Fourier's series:**

$$f(t) = f_{av} + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$f_{av} = \frac{1}{T} \int_0^T f(t) dt$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt, \text{ where } \omega_0 = \frac{2\pi}{T}$$

For an even function,  $a_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \cos n\omega_0 t dt$ , and  $b_n = 0$

For an odd function,  $b_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \sin n\omega_0 t dt$ , and  $a_n = 0$

Filter equations:

## Normalized Butterworth Loss Function, L(s)

n	L(s)
1	(s+1)
2	(s <sup>2</sup> + √2s + 1)
3	(s+1)(s <sup>2</sup> + s + 1)
4	(s <sup>2</sup> + 0.76537s + 1)(s <sup>2</sup> + 1.84776s + 1)

$$\Omega_s = \frac{\omega_s}{\omega_p} \quad \epsilon = \sqrt{10^{0.1L_{\max}} - 1} \quad n \geq \frac{\log_{10} \left( \sqrt{\frac{10^{0.1L_{\min}} - 1}{10^{0.1L_{\max}} - 1}} \right)}{\log_{10}(\Omega_s)}$$

2-port network equations:

$$[T] = \begin{bmatrix} A & -B \\ -C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad D = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

**Transmission Line equations:**


$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$


$$r = \frac{Z_L - Z_c}{Z_L + Z_c}$$

$$\rho = \frac{1 + |r|}{1 - |r|}$$

dB

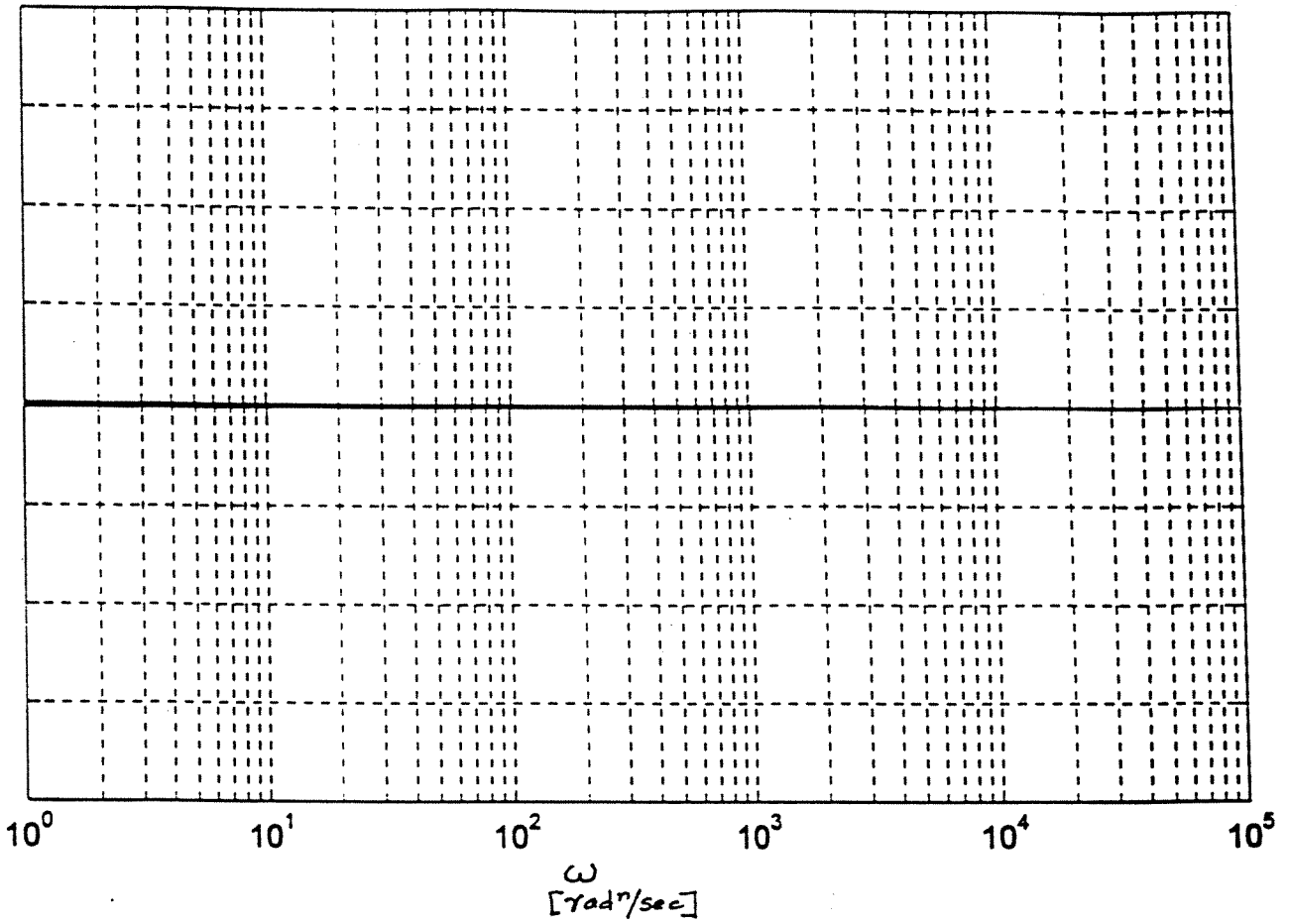

$\theta$

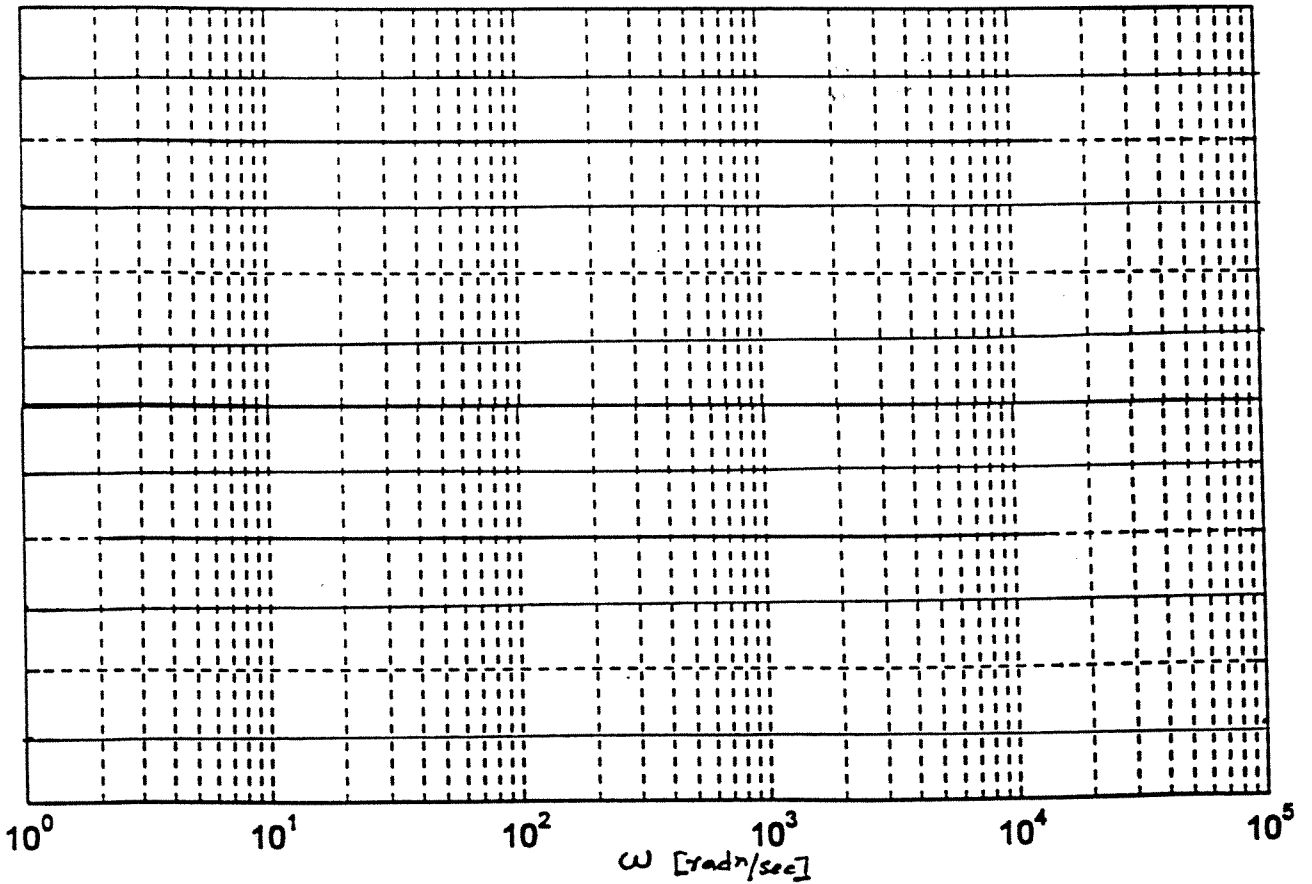

[Please use this graph for question #3, and attach with your answer]