

National Examinations, May 2002

98-Elec-B1, Advanced Circuits Analysis and Design

3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumptions made.
2. Candidates may use one of the approved Casio or Sharp calculators. No programmable calculators are allowed. This is a closed-book examination.
3. Any five questions constitute a complete paper. Only the first five questions, as they appear in your answer book, will be marked.
4. All questions are of equal value; part marks are also indicated.
5. Refer to the appendix for extra information.

Question 1:

In figure-1, the switch was open for a long time. At $t = 0$, the switch is closed.


(a) write the differential equation involving the current $i(t)$ with E , L , C , and R .

[5]

(b) Solve the differential equation to find the current, $i(t)$ at $t > 0$. for the given initial conditions .

[10]

(c) Sketch the waveform of $i(t)$. What is the natural frequency of oscillation of the circuit ?

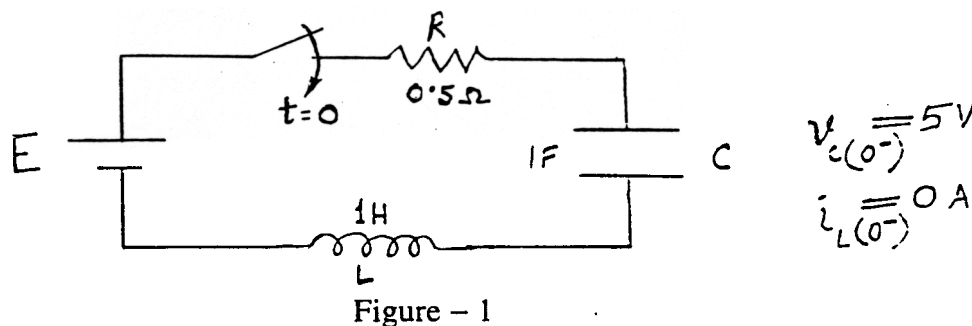

Question 2:

In the block diagram of a control system is shown in figure-2,

(a) calculate the transfer function,

$$H(s) = Y(s) / X(s)$$

[10]

(b) Calculate the poles and zeros of the system. State whether the system will be stable or unstable.


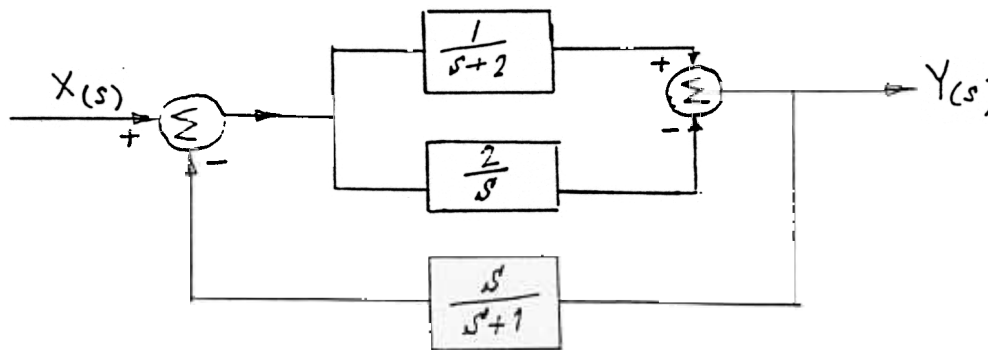


Figure-2

Question 3:

(a) Figure-3 shows the Amplitude of the Bode plot of a network. From this Bode plot, calculate its transfer function, $H(s)$. [10]

(b) From the $H(s)$ obtained in part (a), draw the phase plot. Use the semilog graph attached in the appendix of this question paper. [10]

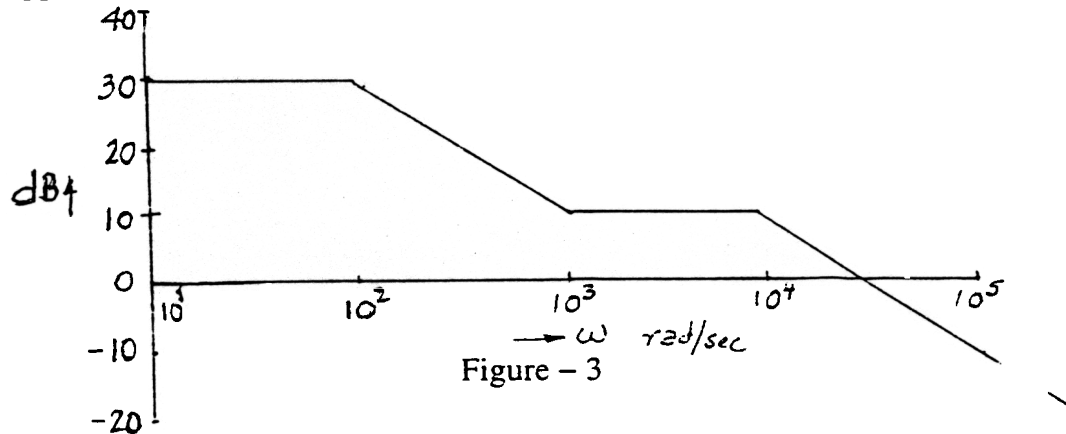

Question 4:

Figure - 4 shows an active low pass filter.

(a) Derive its transfer function, $H(s)$. From this transfer function, write the expression of its cut off frequency, ω_c and gain k of the circuit. [10]

(b) If $\omega_c = 1000$ rad/ sec, gain = 5 and $C = 0.01$ uF, calculate the values of R_1 and R_2 . [10]

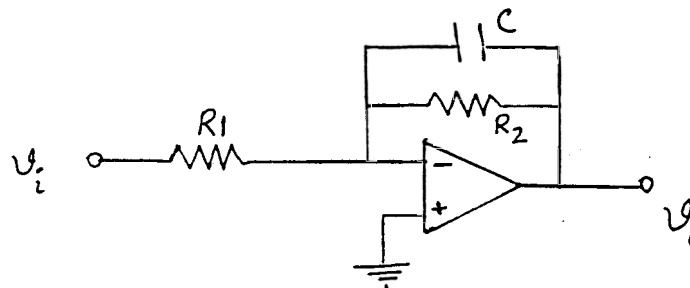


Figure - 4

Question 5:

Calculate the Butterworth low pass transfer function whose 'Brickwall' specifications are shown in figure – 5.

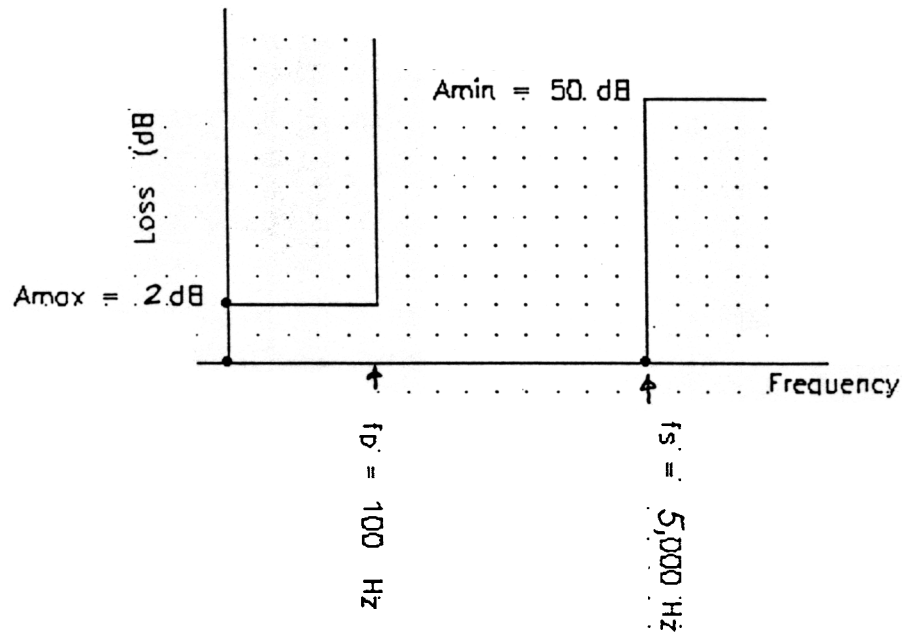


Figure – 5

Question 6:

(a) Calculate the Fourier series of the voltage waveform shown in figure– 6a up to the 5th harmonics. [12]

(b) If the Fourier series of the voltage shown in figure–6a is

$$V_{in} = 1.9 \sin 2094.4t - 0.64 \sin 3141.6t + \sin 4188.8t + \dots$$

calculate the output voltage V_o for the 4th harmonic in figure –6b. [8]

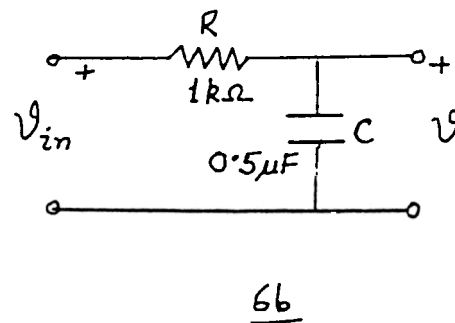
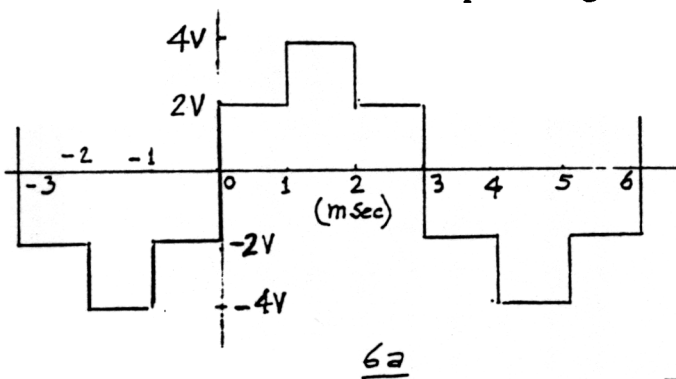
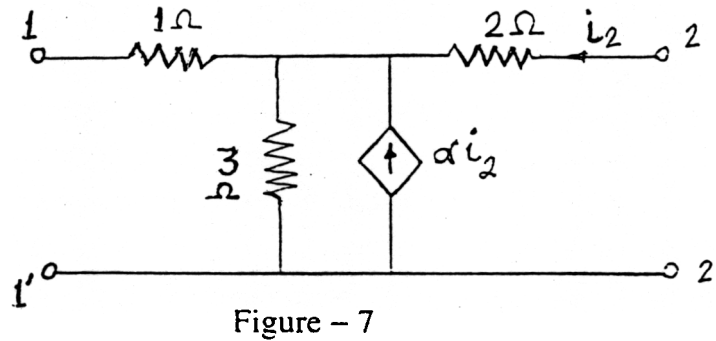


Figure – 6

Question 7:

For the circuit shown in figure – 7, calculate its [z] parameters.

[20]

**Question 8:**

A microwave transmission line at $f = .5$ GHz has $R = 0.5 \Omega /m$, $L = 10^{-8}$ H/m, $C = 10^{-12}$ F/m and $G = 0.0005$ Mho/m.

- Calculate (a) the Characteristic impedance [4]
 (b) the Propagation constant [4]
 (c) what should be its load impedance to eliminate reflection [4]

If the line is terminated by a load impedance of $Z_L = 100 \angle 10^\circ \Omega$, calculate its

- (d) Reflection coefficient, and [4]
 (e) Standing wave ratio [4]

Appendix

Some useful Laplace Transforms:

$f(t)$	→	
$Ku(t)$		
$e^{-at} u(t)$		$1 / (s+a)$
$\sin wt \cdot u(t)$		$w / (s^2+w^2)$
$\cos wt \cdot u(t)$		$s / (s^2+w^2)$
$\frac{df(t)}{dt}$		$sF(s) - f(0^+)$
$\frac{d^2f(t)}{dt^2}$		$s^2F(s) - sf(0^+) - f'(0^+)$
$\int_{-\infty}^{\infty} f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$

Fourier's series:

$$f(t) = f_{av} + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$f_{av} = \frac{1}{T} \int_0^T f(t) dt$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt, \text{ where } \omega_0 = \frac{2\pi}{T}$$

For an even function, $a_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \cos n\omega_0 t dt$, and $b_n = 0$

For an odd function, $b_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \sin n\omega_0 t dt$, and $a_n = 0$

Filter equations:**Normalized Butterworth Loss Function, L(s)**

n	L(s)
1	(s+1)
2	(s ² + √2s + 1)
3	(s+1)(s ² + s + 1)
4	(s ² + 0.76537s + 1)(s ² + 1.84776s + 1)

$$\Omega_s = \frac{\omega_s}{\omega_p} \quad \epsilon = \sqrt{10^{0.1L_{\max}} - 1} \quad n \geq \frac{\log_{10} \left(\sqrt{\frac{10^{0.1L_{\min}} - 1}{10^{0.1L_{\max}} - 1}} \right)}{\log_{10}(\Omega_s)}$$

2-port network equations:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad D = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$[Z] = \begin{bmatrix} \frac{A}{C} & \frac{\Delta T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$$


Transmission Line equations:

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$r = \frac{Z_L - Z_c}{Z_L + Z_c}$$

$$\rho = \frac{1 + |r|}{1 - |r|}$$

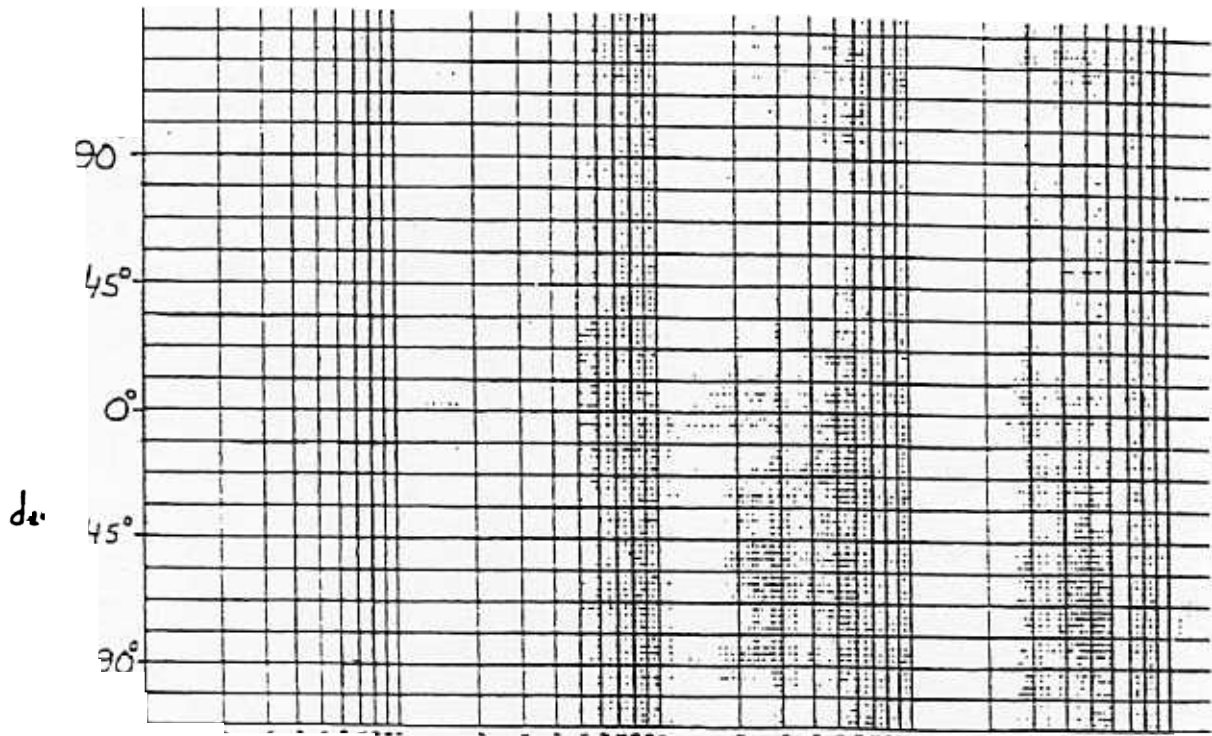

[P as .hi ph f q #4. d tach w h y nsw pape