

National Examinations, May 2003

98-Elec-B1, Advanced Circuits Analysis and Design

3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumptions made.
2. Candidates may use one of the approved Casio or Sharp calculators. No programmable calculators are allowed. This is a closed-book examination.
3. Any five questions constitute a complete paper. Only the first five questions, as they appear in your answer book, will be marked.
4. All questions are of equal value; part marks are also indicated.
5. Refer to the appendix for extra information.

Question 1:

In **Figure-1**, the switch was open for a long time. At $t = 0$, the switch is closed. Using a differential equation approach, (a) write the differential equation involving $v_o(t)$. [10]

(b) Solve the differential equation to find the output voltage, $v_o(t)$ for $t > 0$, if there were on initial charges on C and no initial current in L. [10]

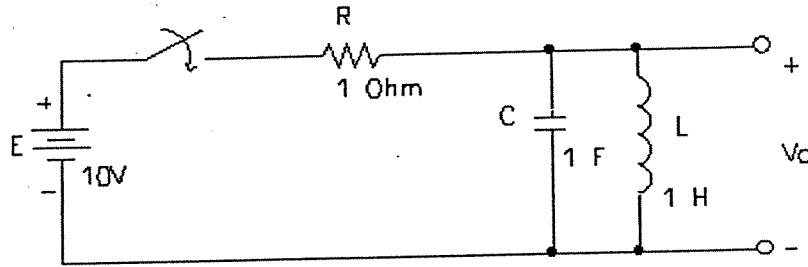


Figure-1

Question 2:

(a) Obtain the transfer function, $T(s) = \frac{Y(s)}{X(s)}$ of the following signal flow block diagram. [10]

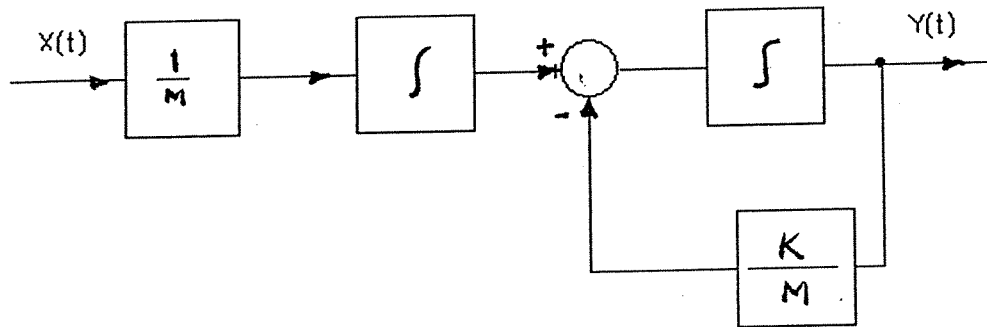


Figure-2

(b) From the transfer function derive the system's differential equation involving, $y(t)$. [4]

(c) If $x(t) = 5 u(t)$, $M = 2$, $K = 1$, and at $t = 0$, $y(t) = 0$, $dy/dt = 10$, solve for $y(t)$. [6]

Question 3:

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{2(s+5)}{s(s+10)^2}$$

(a) If the transfer function of a circuit is
draw the Bode plot (amplitude and phase), showing clearly the break frequencies. Please use the graph paper provided in the appendix in page-10. [12]

(b) An Amplitude plot in dB of $H(s)$ is shown in Figure – 3. Obtain the transfer function, $H(s)$. [8]

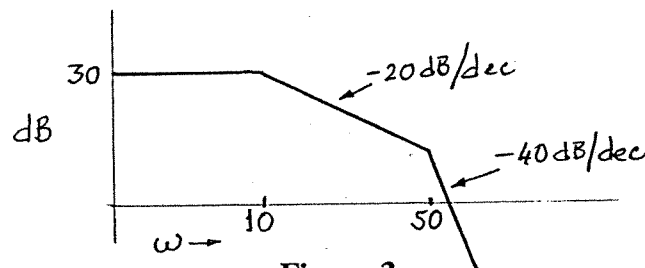


Figure-3

Question-4:

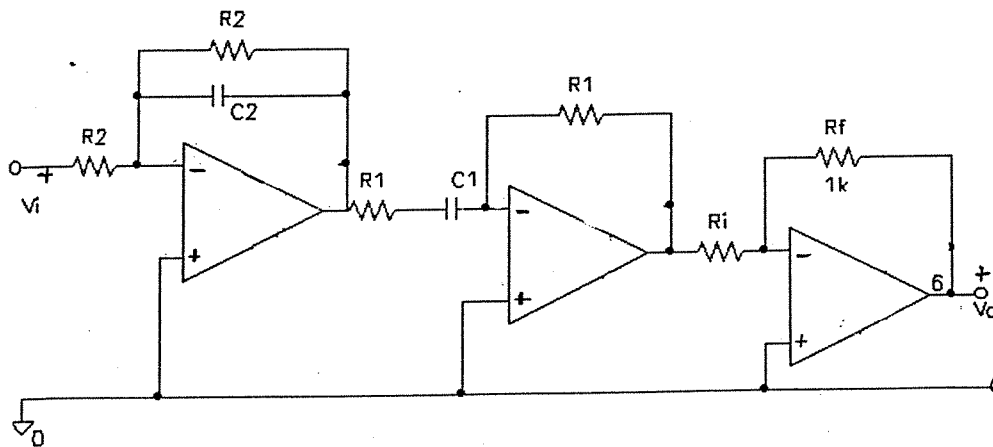


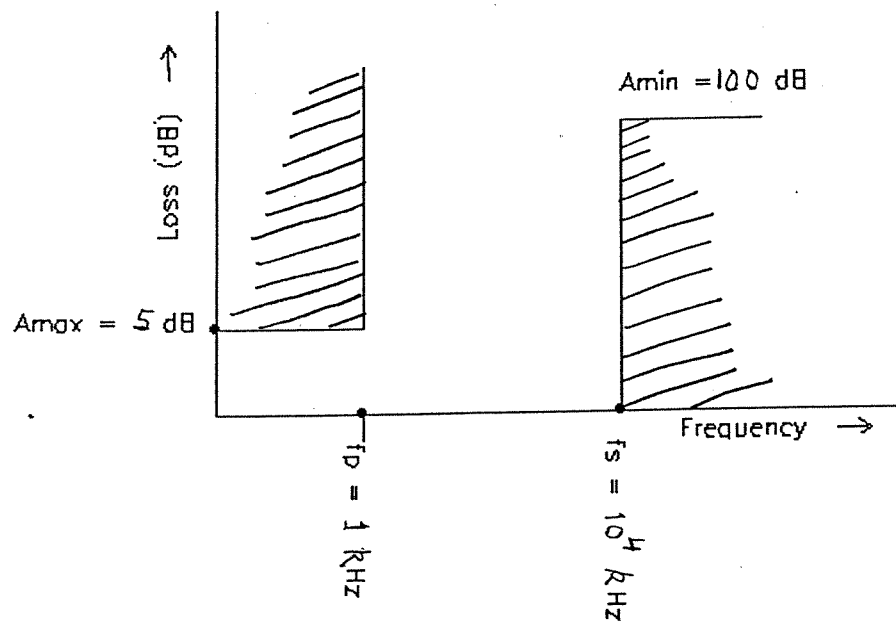
Figure -4

Figure – 4 shows an active filter circuit.

- (a) Derive the expression of its transfer function $H(s)$ in terms of ω , capacitors and resistances shown in the circuit. [8]
- (b) If $R_1=5k\Omega, C_1=0.1\mu F, R_2=1k\Omega, C_2=0.01\mu F, R_i=1k\Omega, R_f=100k\Omega$, find ω_o and Gain at ω_o . [8]
- (c) State what type of filter this is. [4]

Question 5:

Obtain the transfer function, $H(s)$ of a Butterworth filter to approximate the following 'Brickwall' specifications.

**Figure -5**

The relevant filter equations are provided in the appendix.

[20]

Question 6:

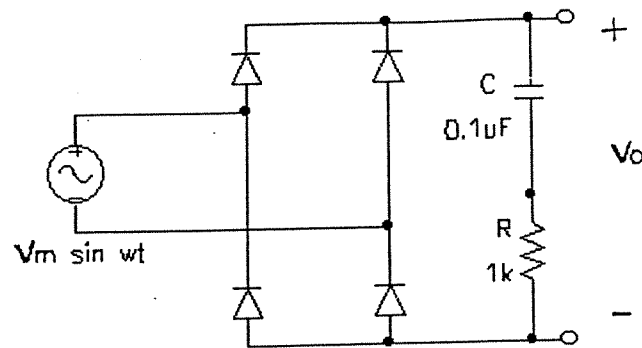


Figure - 6

- (i) For the circuit shown in **Figure – 6**, calculate the dc and the fundamental component of the in the output voltage, V_o , if $V_m = 10\text{v}$ and frequency of supply is 60 Hz. [10]
- (ii) Calculate the power dissipation in the RC load for the fundamental component of V_o . [10]

Question 7:

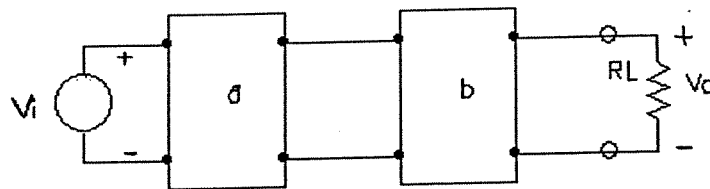


Figure-7

Two port networks [a] and [b] are cascaded as shown in figure-7. If the parameters of the 2-port networks are given as shown below.

$$[Z_a] = \begin{bmatrix} 4 & 3 \\ 2 & 2.5 \end{bmatrix} \Omega \quad \text{and} \quad [Y_b] = \begin{bmatrix} 8 & -2 \\ 1 & 5 \end{bmatrix} S$$

- (a) Calculate the overall T - parameters of the circuit. [10]
- (b) If $R_L = 2\Omega$, find the voltage ratio V_o/V_i of the circuit. [10]

Question 8:

A transmission line has the following parameters at 2 GHz:

$$L = 8 \text{ nH/m} \quad R = 1.1 \text{ } \Omega/\text{m} \quad G = 0.2 \times 10^{-3} \text{ mho/m} \quad C = 0.1 \text{ pF/m}$$

- Calculate (i) the Characteristic impedance of the line,
(ii) the propagation constant,
(iii) the load impedance to eliminate the reflection from the load.
(iv) if the line is terminated with a load impedance of $50 - j 25 \text{ } \Omega$,
calculate its reflection coefficient, and the standing wave ratio.

[20]

Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
Ku(t)		K / s
e ^{-at} u(t)		1 / (s+a)
sin wt .u(t)		w / (s ² +w ²)
cos wt . u(t)		s / (s ² +w ²)
$\frac{df(t)}{dt}$		s F(s) - f(0 ⁻)
$\frac{d^2 f(t)}{dt^2}$		s ² F(s) - s f(0 ⁻) - f'(0 ⁻)
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$

Fourier's series:

$$f(t) = f_{av} + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$f_{av} = \frac{1}{T} \int_0^T f(t) dt$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt, \text{ where } \omega_0 = \frac{2\pi}{T}$$

$$\text{For an even function, } a_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \cos n\omega_0 t dt, \text{ and } b_n = 0$$

$$\text{For an odd function, } b_n = \frac{4}{T} \int_0^{\frac{T}{2}} f(t) \sin n\omega_0 t dt, \text{ and } a_n = 0$$

Filter equations:

Normalized Butterworth Loss Function, L(s)

n	L(s)
1	(s+1)
2	(s ² + √2s + 1)
3	(s+1)(s ² + s + 1)
4	(s ² + 0.76537 s + 1)(s ² + 1.84776 s + 1)

$$\Omega_s = \frac{\omega_s}{\omega_p} \quad \epsilon = \sqrt{10^{0.1L_{\max}} - 1} \quad n \geq \frac{\log_{10} \left(\sqrt{\frac{10^{0.1L_{\min}} - 1}{10^{0.1L_{\max}} - 1}} \right)}{\log_{10}(\Omega_s)}$$

2-port network equations

	z-Parameters	y-Parameters	h-Parameters	t-Parameters
z-Parameters	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{y_{22}}{\Delta y} & \frac{-y_{12}}{\Delta y} \\ \frac{-y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{-h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{11}}{t_{21}} & \frac{\Delta t}{t_{21}} \\ \frac{1}{t_{21}} & \frac{t_{22}}{t_{21}} \end{bmatrix}$
y-Parameters	$\begin{bmatrix} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & \frac{-h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{22}}{t_{12}} & \frac{-\Delta t}{t_{12}} \\ \frac{-1}{t_{12}} & \frac{t_{11}}{t_{12}} \end{bmatrix}$
h-Parameters	$\begin{bmatrix} \frac{\Delta z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ \frac{-z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{y_{11}} & \frac{-y_{12}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & \frac{\Delta y}{y_{11}} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{t_{12}}{t_{22}} & \frac{\Delta t}{t_{22}} \\ \frac{-1}{t_{22}} & \frac{t_{21}}{t_{22}} \end{bmatrix}$
t-Parameters	$\begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix}$	$\begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-\Delta y}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix}$	$\begin{bmatrix} \frac{-\Delta h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \end{bmatrix}$	$\begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix}$

2-port network equations (continued):

$$[T] = \begin{bmatrix} A & -B \\ -C & D \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad D = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$



Transmission Line equations:

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$r = \frac{Z_L - Z_c}{Z_L + Z_c}$$

$$\rho = \frac{1 + |r|}{1 - |r|}$$

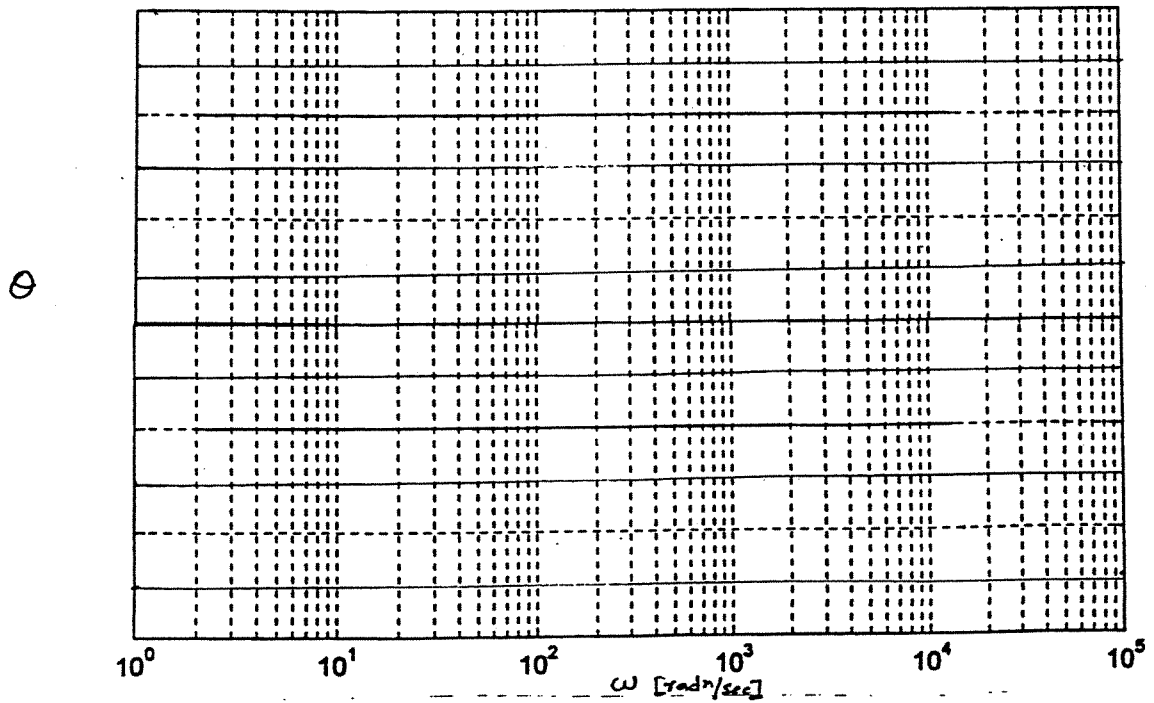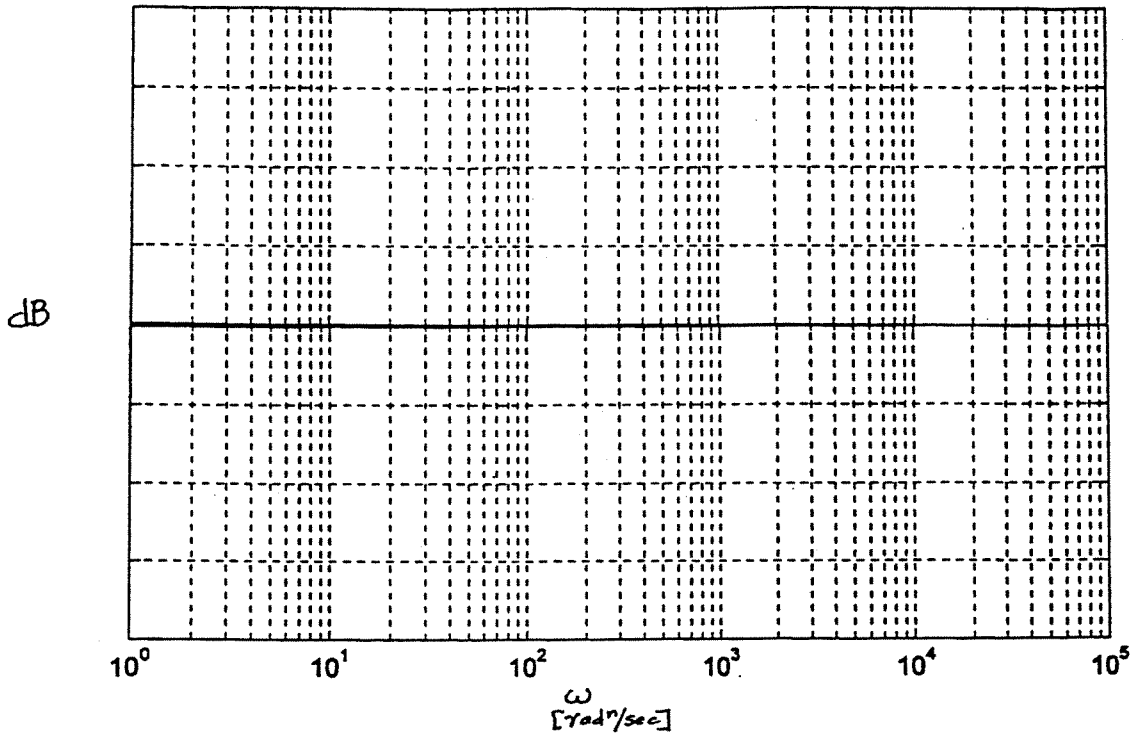

[Please use this graph for question #3, and attach with your answer]