

PROFESSIONAL ENGINEERS ONTARIO
National Examinations - May 2002
98-Mec-A6, Electrical and Electronics Engineering
Mechanical Engineering

3 hours duration

NAME [print]:

SIGNATURE:

NOTES:

- [1] If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumptions made.
- [2] Candidates may use one of two calculators, the Casio or Sharp approved models. This is a closed book examination.
- [3] Any five questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked.
- [4] All questions are of equal value.
- [5] The candidate is required to sign this examination paper and submit it with the solution booklets.
- [6] $\pi = 3.14159$
 $1 \text{ hp} = 746 \text{ W}$
 $\mu_0 = 4\pi \times 10^{-7} \text{ H m}^{-1}$

Front Page

QUESTION 1

Consider the transistor circuit shown in Figure 1. All transistors can be assumed to be identical with a dc current gain β .

Calculate the current transfer ratio for the circuit, I_2 / I_1 , as a function of β .

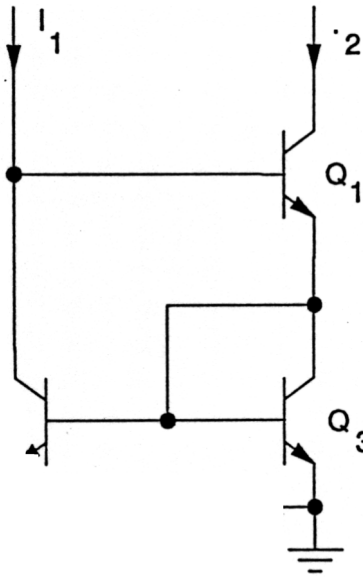


Figure 1 Transistor Circuit

QUESTION 2

An industrial load is represented in Figure 2 by $R = 6\Omega$ and $X_L = 8\Omega$. The load voltage is $250\angle 0^\circ$ V.

- Calculate the load current, power, reactive power and power factor.
- Calculate the generator voltage V_G required at the input end of the transmission line (represented by the series impedance $Z_T = (1 + j3)\Omega$) and the power lost in transmission P_T .
- If capacitor $X_C = 12.5\Omega$ is connected in parallel by closing switch S, calculate I_C , the new load current I , and the new power factor. Show V , I_L , I_C , and I on a phasor diagram.
- Calculate the new generator voltage and the new transmission power loss.
- What two advantages do you see for improving the power factor by adding a parallel capacitor?

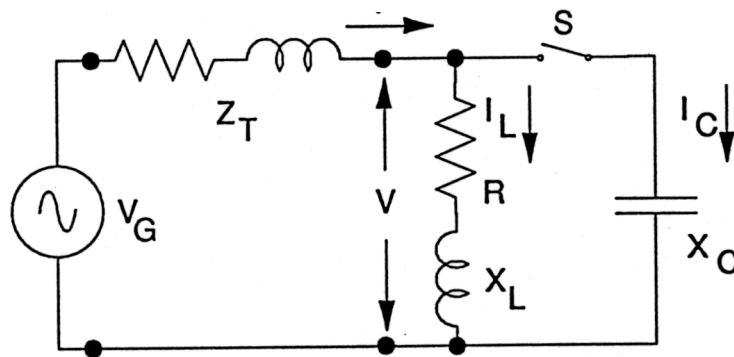


Figure 2 Industrial Load

QUESTION 3

Consider the magnetic circuit of a transformer shown in Figure 3. Infinite relative permeability can be assumed for the iron core.

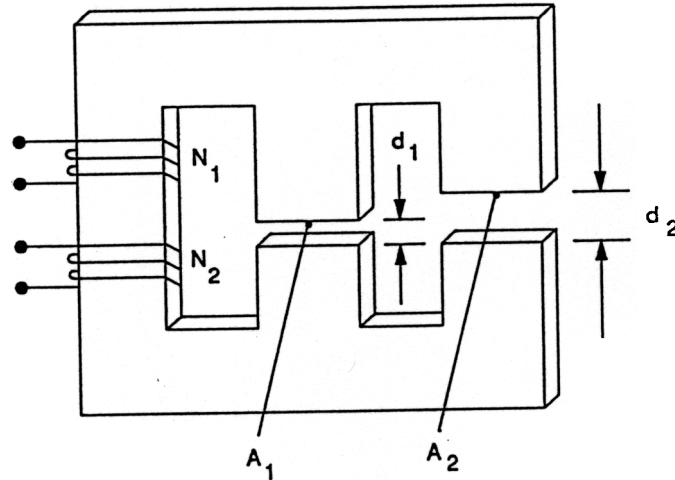


Figure 3 Transformer

The following specifications apply.

d_1	$3.77 \times 10^{-2} \text{ m}$	A_1	0.02 m^2
d_2	$7.54 \times 10^{-2} \text{ m}$	A_2	0.02 m^2
N_1 [primary]	200 turns	N_2 [secondary]	20 turns

When a dc voltage equal to 10 mV is applied to the primary, the measured primary current is 100 mA. When a dc voltage of 0.1 mV is applied to the secondary winding, the measured secondary current is 100 mA.

Assume that leakage inductances and eddy current and hysteresis losses are negligible; consider an operating frequency of 1000 Hz.

- Draw the equivalent circuit of the transformer, referred to the primary and calculate component values.
- A transducer, with an impedance of 0.078Ω , is connected across the secondary of the transformer; an amplifier is connected to the primary. Calculate the output impedance of the amplifier to give maximum power transfer to the load.

QUESTION 4

Design a combinational logic circuit to meet the following specifications:

Input: A
3-bit binary number, $A_2A_1A_0$
[$A_2 = \text{MSB}$; $A_0 = \text{LSB}$]

Output: Y
6-bit binary number equal to the square of the input number
 $Y_5Y_4Y_3Y_2Y_1Y_0$
[$Y_5 = \text{MSB}$; $Y_0 = \text{LSB}$]

A block diagram of the logic circuit is shown in Figure 4.

- [a] Develop the truth table for the logic circuit.
- [b] Write Boolean algebra expressions for the outputs as a function of the inputs and simplify where possible.
- [c] Design the gate array to implement your design.
Only 2-input NOR gates are available.

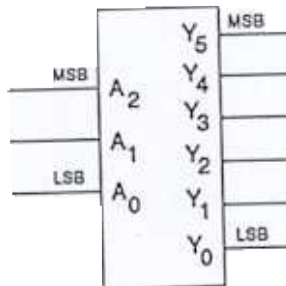


Figure 4 Block Diagram of Combinational Logic Circuit


QUESTION 5

Consider the RC circuit shown in Figure 5[a]. The switch S_1 is closed at time $t=0$, connecting the dc supply V_1 to the network.


- [a] Derive an expression for the transfer function of the circuit V_o/V_1 in the time domain.
- [b] Sketch the transfer function for a time interval of 5 time constants.

The RC circuit is reconfigured as shown in Figure 5[b]. An ac voltage source of variable frequency v_i is connected to the input.

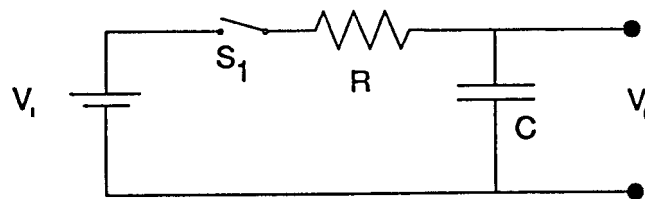- [c] Derive an expression for the transfer function of the circuit v_o/v_i in the frequency domain.
- [d] Sketch the magnitude of the transfer function for a frequency range of 4 decades centered at the corner frequency of the circuit.



[a]

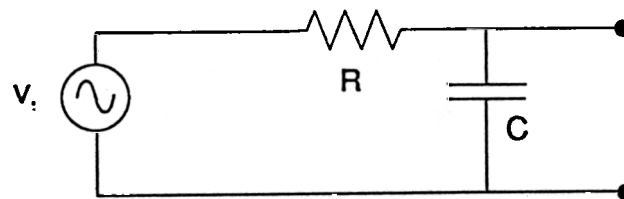

[b]

Figure 5: RC Circuit, [a] dc test, [b] ac test

QUESTION 6

Consider the circuit shown in Figure 6. Assume an ideal operational amplifier with infinite bandwidth and infinite open loop gain.

- [a] Use the straight line approximation technique to sketch a plot of the magnitude of V_O / V_I in db versus \log_{10} of frequency for a frequency range of 0.001 Hz to 10 MHz. Clearly indicate all gain levels, corner frequencies and unity gain points. Show calculations of the data used to plot your graph.
- [b] A signal generator is connected to the input of the circuit.
- [1] A sinusoidal wave, of frequency 0.01 Hz, is selected for input to the circuit. What is the function of the circuit at this frequency? Write an expression for the transfer function of the circuit in the time domain.
 - [2] A sinusoidal wave, of frequency 1000 Hz, is selected for input to the circuit. What is the function of the circuit at this frequency? Write an expression for the transfer function of the circuit in the time domain.
 - [3] A sinusoidal wave, of frequency 1 MHz, is selected for input to the circuit. What is the function of the circuit at this frequency? Write an expression for the transfer function of the circuit in the time domain.

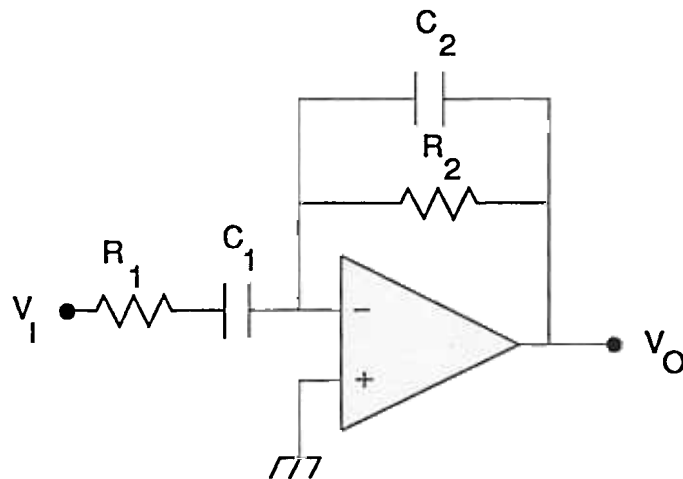


Figure 6 Circuit Schematic

RESISTORS		CAPACITORS	
R_1	160 kohm	C_1	1.0 μ F
R_2	16 Mohm	C_2	1 pF
COMPONENT LIST			

QUESTION 7

A novel type of DC machine can be designed using a spoke-like rotor with current carrying conductors arranged in a radial fashion, as shown in Figure 7. Current is fed radially through the rotor spokes via two ring shaped carbon brushes. The rotor lies in the horizontal plane and is situated in a uniform vertical magnetic field.

The rotor has an outer radius, $R_2 = 0.2$ m, and an inner radius, $R_1 = 0.05$ m, and consists of 8 conductors. The flux density, B , is 0.5 T.

- [a] If the rotor runs at a speed of $n = 3000$ rpm, find the magnitude of the emf, e , generated between the brushes.
- [b] If a total current of 500 A flows radially between the brushes, calculate the torque that the rotor will be subjected to and determine the output horsepower of the machine.

HINT: As a starting point, consider a small radial element of length dr located at a distance r from the centre of rotation.

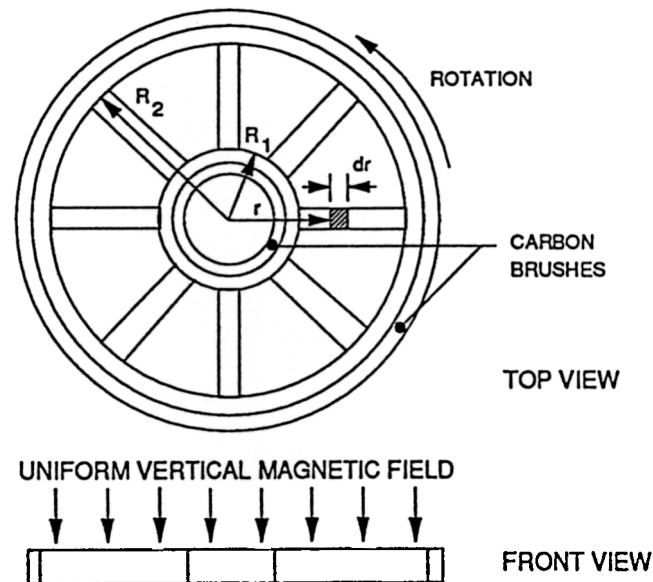


Figure 7 DC Machine

QUESTION 8

The results of no-load and blocked-rotor tests conducted on a three-phase wye-connected induction motor are as follows:

No-load test:

line-to-line voltage: 400V

input power: 1770W

input current: 18.5A

friction and windage loss: 600W

Blocked-rotor test:

line-to-line voltage: 45V

input power: 2700W

input current: 63A

- [a] Sketch the equivalent circuit of the induction motor and identify all parameters.
- [b] Determine the parameters of the equivalent circuit of the induction motor.