

December 2007 NATIONAL EXAMS

98 – ELEC – B8

Switched Mode Power Supply Design

3 Hours Duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper a clear statement of any assumption made;
2. “Closed-Book” – Candidates may use one of two calculators, a Casio or Sharp
3. Any five questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked;
4. All questions are of equal value

Question 1

- a) What is a line impedance stabilization network (LISN)?
- b) What is the difference between a Faraday screen and safety screen in a switching transformer?
- c) Why is the i^2t rating of a fuse an important selection criterion?
- d) Describe the difference between differential-mode interference and common-mode interference.

Question 2

- a) Why are capacitive input filters often used for direct-off-line switch-mode supplies?
- b) What is the typical power factor of a capacitive input filter, and why is it relatively poor?
- c) Why must a true wattmeter be used for measuring input power?
- d) Why is line inrush-current limiting required with capacitive input filter circuits are employed?

Question 3

- a) Why is output over-voltage protection often considered necessary?
- b) Name three types of over-voltage protection in common use.
- c) Describe what is meant by crowbar over-voltage protection.
- d) Describe the problems normally encountered with a fast-acting crowbar protection circuit.

Question 4

- a) Explain what is meant by the term “snubber network.”
- b) Explain the two major functions of a typical snubber network.
- c) Why is a large snubber capacitor undesirable?
- d) Describe a low-loss snubber technique that may be used in place of the conventional *RC* snubber network.

Question 5

- a) Discuss the major disadvantage of switch-mode power supplies compared with the older linear regulator types.
- b) Is the design of the output filter the only most important factor in reducing output ripple noise?
- c) Why are power output filters often relatively ineffective in dealing with high-frequency noise?
- d) What is the difference between common-mode and differential-mode noise filters?

Question 6

- a) Why does operation in parallel for constant-voltage power supplies present a problem?
- b) Explain the major disadvantages of master-slave operation.
- c) How can we achieve forced current sharing for parallel operation ?
- d) What is meant by parallel redundant operation?

Question 7

- a) Explain the basic operation of a fly-back converter.
- b) Explain the major parameters that control the selection of the switching transistor in a fly-back converter.
- c) What is the steady state input / output voltage and current transfer function of a fly-back converter?
- d) What parameters of the fly-back converter control the selection of the output capacitors?